Hands-on hardware tutorial

Nele Mentens

Selected Areas in Cryptography Summer School

August 13, 2019, Waterloo, Canada

Outline

LEUVEN

- Implementation platforms + design flows
- Introduction to VHDL
- Hardware tutorial

- Implementation platforms + design flows
- Introduction to VHDL
- · Hardware tutorial


SAC summer school, 2019, Waterloo, Canada

Implementation platforms

LEUVEN

- Microprocessor
- FPGA = Field-Programmable Gate Array
- ASIC = Application-Specific Integrated Circuit

Microprocessor architecture

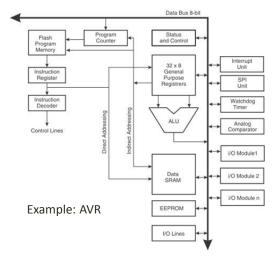


The CPU is the heart of a microprocessor and contains a.o.:

- ALU (Arithmetic Logic Unit)
- register file
- program memory

SAC summer school, 2019, Waterloo, Canada

Microprocessor design flow


LEUVEN

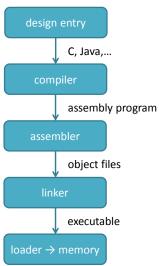

- The hardware architecture of a microprocessor is fixed
- The code describes what should be executed on the fixed hardware
- The instructions end up in the program memory

FPGA architecture



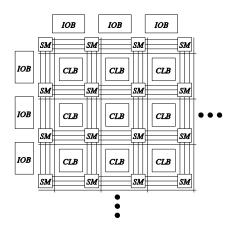

Basic components:


- CLB = Configurable Logic Block
 - CLBs consist of slices.
 - Slices consist of
 - Look-Up Tables (LUTs),
 - · Multiplexers,
 - Flip-Flops (FFs),
 - · Carry logic.
- SM = Switch Matrix
- IOB = Input/Output Block

SAC summer school, 2019, Waterloo, Canada

FPGA slice

LEUVE


basic content of a slice

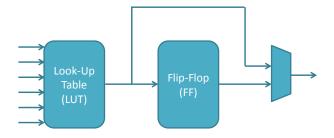

FPGA switch matrix

LEUVE


basic principle of a switch matrix

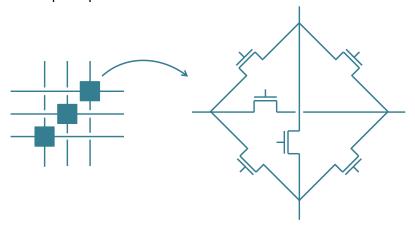

SAC summer school, 2019, Waterloo, Canada

FPGA design flow


LEUVEN

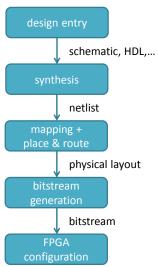

- The hardware architecture of an FPGA is configurable
- The code describes the hardware that we need
- The bitstream ends up in the configuration memory
- The area is measured in terms of occupied LUTs, flip-flops, dedicated hardware blocks

ASIC architecture



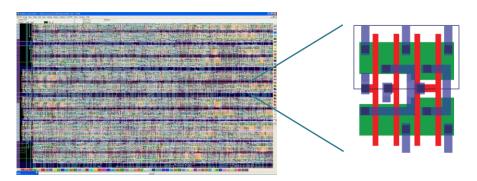


Basic components:

- · Standard cells from a standard cell library
 - Logic cells and sequential cells


SAC summer school, 2019, Waterloo, Canada

ASIC design flow


LEUVEN

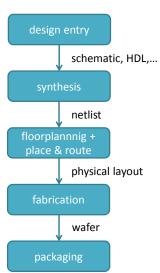

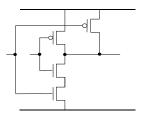- The hardware architecture of an ASIC is defined by the designer
- The code describes the hardware that we need
- The GDS file contains the physical information that goes to the foundry
- The area is measured in terms of the number of equivalent NAND gates (Gate Equivalent = GE)



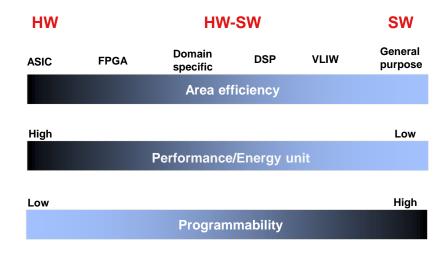SAC summer school, 2019, Waterloo, Canada



SAC summer school, 2019, Waterloo, Canada


Outline

- LEUVE
- Implementation platforms + design flows
- Introduction to VHDL
- Hardware tutorial

Introduction to VHDL Standard

LEUVE

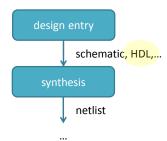- VHDL (VHSIC Hardware Description Language)
 - VHSIC = Very High Speed Integrated Circuit
- International standard
 - First standard: IEEE 1076-1987
 - Most recent update: IEEE 1076-2008
- Used for both ASIC and FPGA design



SAC summer school, 2019, Waterloo, Canada

Introduction to VHDL Hardware vs. software

- LEUVEN
- Description language for hardware ≠ programming language
- Programming language (e.g. C):
 - hardware = processor
 - hardware is already designed, implemented and fabricated
 - code: describes how the hardware will be used
 - code is compiled for a specific processor
- Hardware description language (e.g. VHDL)
 - hardware = FPGA or ASIC design
 - hardware is designed
 - code: describes which hardware will be designed
 - code is synthesized for a specific FPGA or ASIC technology
 - example: c <= a and b; e <= c or d; e <= c or d; c <= a and b; c <= a and b; e <= c or d; c <= a and b; e <= c or d; c <= a and b; e <= c or d; c <= a and b; e <= c or d; e <= c o

Introduction to VHDL **Entities and architectures**

- The VHDL code of each component consists of
 - an interface description: entity,
 - a behavioral description: architecture.


```
· Example:
                                             entity and_or_gate is
                                                           a, b, d: in bit;
                                                  port(
   а
                                                           e: out bit);
                                             end and_or_gate;
                                             architecture arch of and_or_gate is
                                                  signal c: bit;
                                             begin
                                                  c \le a and b;
                                                  e \le c \text{ or } d:
                                             end arch;
```

SAC summer school, 2019, Waterloo, Canada

Introduction to VHDL Hierarchy

- There is hierarchy when a component contains an instantiation of another component.

Hierarchy can be built in.

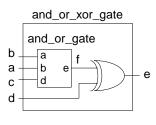

```
entity and_or_xor_gate is
     port(a, b, c, d: in bit;
          e: out bit);
end and_or_xor_gate;
architecture arch of and_or_xor_gate is
    component and_or_gate is
          port(a, b, d: in bit;
               e: out bit);
    end component;
     signal f: bit;
begin
     inst_and_or_gate: and_or_gate
          port map(a => b,
                    b \Rightarrow a
                    d => c,
     e \le d xor f;
end arch;
```

Introduction to VHDL Hierarchy


LEUVE

```
entity and_or_xor_gate is
    Hierarchy can be built in.
                                                port(a, b, c, d: in bit;
    There is hierarchy when a
                                                     e: out bit);
    component contains an
                                            end and_or_xor_gate;
    instantiation of another
                                            architecture arch of and_or_xor_gate is
    component.
                                                component and_or_gate is
                                                     port(a, b, d: in bit;
         and_or_xor_gate
                                                          e: out bit);
        and_or_gate
                                                 end component;
                                                signal f: bit;
    b
                                            begin
    а
                                                inst_and_or_gate: and_or_gate
    С
                                                     port map(a \Rightarrow b,
    d
                                                               b => a
                                                               d => c,
inst_and_or_gate: and_or_gate
                                                               e \Rightarrow f;
    port map(b, a, c, f);
                                                 e <= d xor f;
                                            end arch;
             order must
             be correct
```

SAC summer school, 2019, Waterloo, Canada

Introduction to VHDL bit vs. std_logic

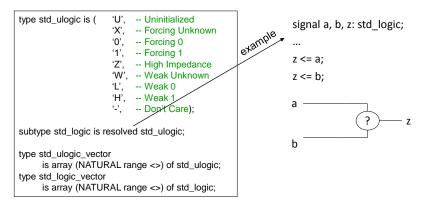
 The package "std_logic_1164" in library "ieee" contains a.o. the types "std_ulogic" en "std_logic", consisting of 9 values (instead of 2 for "bit")



It is advised to always use "std_logic" instead of "bit"

Introduction to VHDL Concurrent and sequential statements

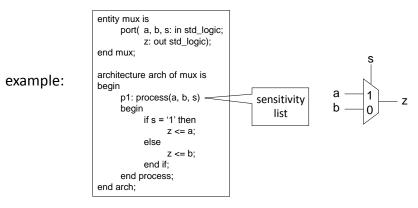- Concurrent statements: are implement in parallel and executed at the same time
- Sequential statements: can only occur in a process




SAC summer school, 2019, Waterloo, Canada

Introduction to VHDL Storage elements

LEUVEN

• D-flipflop:

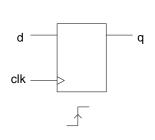


```
library ieee;
use ieee.std_logic_1164.all;

entity dff is
    port( d, clk: in std_logic;
        q: out std_logic);
end dff;

architecture arch of dff is
begin
    store: process(clk)
    begin
    if clk'event and clk = '1' then
        q <= d;
    end if;
    end process;
end arch;
```

Introduction to VHDL Storage elements

D-flipflop with asynchronous reset:

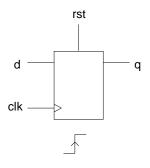


```
use ieee.std_logic_1164.all;
entity dff is
     port(d, clk, rst: in std_logic;
           q: out std_logic);
end dff;
architecture arch of dff is
begin
     store: process(rst, clk)
     begin
           if rst = '1' then
                 q <= '0';
           elsif clk'event and clk = '1' then
                 q \le d;
           end if;
     end process;
end arch;
```

SAC summer school, 2019, Waterloo, Canada

Introduction to VHDL Storage elements

D-flipflop with synchronous reset:

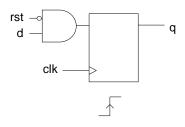


```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
     port( d, clk, rst: in std_logic;
           q: out std_logic);
end dff;
architecture arch of dff is
begin
     store: process(clk)
     begin
           if clk'event and clk = '1' then
                 if rst = '1' then
                       q <= '0';
                 else
                       q <= d;
                 end if;
           end if;
     end process;
end arch;
```

SAC summer school, 2019, Waterloo, Canada

VIEW NIVERSI E

Introduction to VHDL Storage elements

• D-flipflop with enable:

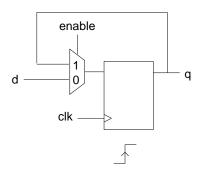


```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
     port( d, clk, enable: in std_logic;
           q: out std_logic);
end dff;
architecture arch of dff is
begin
     store: process(clk)
     begin
           if clk'event and clk = '1' then
                 if enable = '1' then
                       q \le d;
                 end if;
           end if;
     end process;
end arch;
```

SAC summer school, 2019, Waterloo, Canada

Introduction to VHDL Modules with parameters

LEUVEN

Register with a parameterizable width:

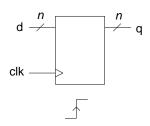

```
library ieee;
use ieee.std_logic_1164.all;
entity ffn is
     generic(size: integer:=4);
     port( clk: in std_logic;
           d: in std_logic_vector(size-1 downto 0);
           q: out std_logic_vector(size-1 downto 0));
end ffn;
architecture arch of ffn is
begin
     p: process(clk)
     begin
           if clk'event and clk = '1' then
                 q \le d;
           end if;
     end process;
end arch;
```

Introduction to VHDL Simulation

- A VHDL module can be simulated with a testbench:
 - Also written in VHDL
 - No ports in the entity
 - Containing an instantiation of the device under test (DUT)
- Input signals are applied internally in the testbench
- · Output signals are evaluated
 - Through waveforms in a simulation window
 - In a text file
 - By comparing the behavior of the DUT to a golden reference model
 - in VHDL, directly in the testbench
 - in another programming language (e.g. C)

DUT

SAC summer school, 2019, Waterloo, Canada

Introduction to VHDL Example

LEUVEN

```
entity invert is

port(
a: in bit;
b: out bit);
end invert;

architecture arch of invert is begin
b <= not a;
end arch;
```

```
invert b -
```

```
entity test_invert is
end test_invert;
architecture arch of test_invert is
          signal a, b: bit;
           component invert is
                                 a: in bit;
                      port(
                                 b: out bit);
          end component;
begin
           inst_invert: invert
                      port map(a, b);
           p: process
           begin
                      a <= '0';
                      wait for 10 ns;
                      a <= '1';
                      wait for 10 ns;
                      wait;
           end process;
end arch;
```


- Implementation platforms + design flows
- Introduction to VHDL
- Hardware tutorial

SAC summer school, 2019, Waterloo, Canada

Hardware tutorial

LEUVEN

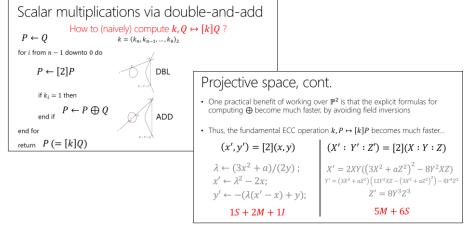
Remember from Monday: "Introduction to elliptic curve cryptography", Craig Costello



Hardware tutorial

LEUVEN

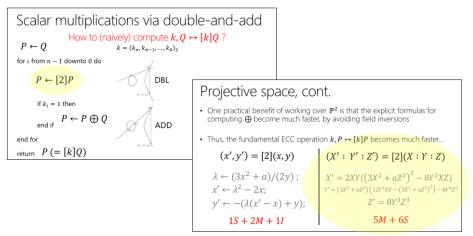In this tutorial, we will implement elliptic curve point doubling using projective coordinates



SAC summer school, 2019, Waterloo, Canada

Hardware tutorial

LEUVEN

The basic operations we need to implement, are:

- Modular addition
- · Modular subtraction
- Modular multiplication
- Modular squaring

Scalar multiplications via double-and-add How to (naively) compute $k,Q\mapsto [k]Q$?

P $\leftarrow Q$ for i from n-1 downto 0 do

P $\leftarrow [2]P$ if $k_i=1$ then

end if

P $\leftarrow P\oplus Q$ end for

return P (=[k]Q)ADD

Projective S• One practical ber computing \oplus bev

• Thus, the fundam (x',y')=[x',y']

Projective space, cont.

- One practical benefit of working over \mathbb{P}^2 is that the explicit formulas for computing \oplus become much faster, by avoiding field inversions
- Thus, the fundamental ECC operation $k, P \mapsto [k]P$ becomes much faster...

(x',y') = [2](x,y) $\lambda \leftarrow (3x^2 + a)/(2y);$ $x' \leftarrow \lambda^2 - 2x;$ $y' \leftarrow -(\lambda(x' - x) + y);$ 1S + 2M + 1I (X' : Y' : Z') = [2](X : Y : Z) $X' = 2XY((3X^2 + aZ^2)^2 - 8Y^2XZ)$ $Y' = (3X^2 + aZ^2)(12Y^2XZ - (3X^2 + aZ^2)^2) - 8Y^4Z^2$ $Z' = 8Y^3Z^3$ 5M + 6S

Hardware tutorial

LEUVEN

The basic operations we need to implement, are:

- · Modular addition
- · Modular subtraction
- · Modular multiplication
- Modular squaring

The datapath will consist of very basic modules for these operations

We will not design a dedicated modular squaring module; squaring can be done using the modular multiplication module


In order to store the intermediate values, a register file is needed

A finite state machine (FSM) will control the datapath and the register file

SAC summer school, 2019, Waterloo, Canada

Hardware tutorial

LEUVE

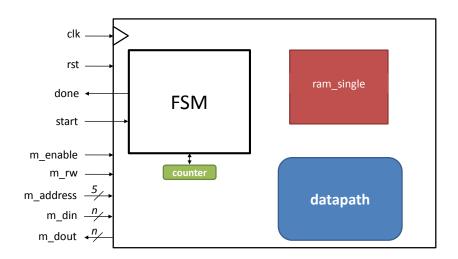

Hardware tutorial

LEUVEN

- 4-bit adder
- n-bit adder
- 4-bit modular adder
- EXERCISE: n-bit modular adder
- n-bit modular adder/subtracter
- n-bit modular constant multiplier (multiplication by 5)
- EXERCISE: n-bit modular multiplier
 - through consecutive additions
- EXERCISE: n-bit modular multiplier
 - through left-to-right modular double-and-add
- single-port memory unit
- EXERCISE: elliptic curve point doubling

SAC summer school, 2019, Waterloo, Canada

Hardware tutorial

LEUVE

- For each module, the VHDL code for the module and the VHDL code for the testbench are given
- Where it says EXERCISE, the VHDL code for the module needs to be completed
- The tutorial will cover only behavioral simulation, i.e. pre-synthesis simulation based on the VHDL design without taking into account gate delays.

